

Digital Synthesizer - MVP

Devlin Ih and Neel Dhulipala

Overview

The goal of this project was to make a dual-channel digital synthesizer. The input consists of three buttons, with one that selects a waveform for both channels and the other two being keys with fixed pitches. The output of our module is a PWM signal that is read by a [Digilent PmodAMP2](#) as an audio signal, which can be outputted by a speaker. Figure 1 displays the block diagram of our circuit.

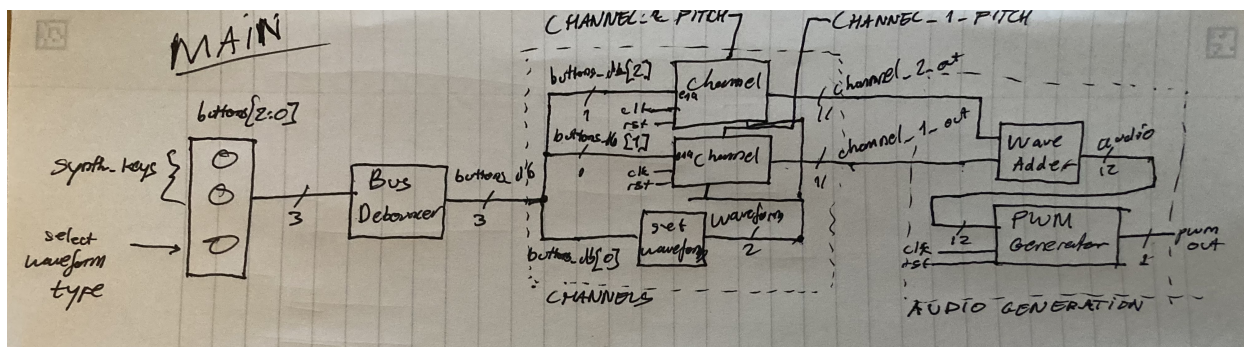


Figure 1: Block diagram of module

In this report, we will describe each aspect of the module.

Audio PWM Generator

The `audio_pwm_generator` module takes in our 12 bit audio signal and modulates it out as a 1-bit PWM signal. Its input ports are `[11:0] audio`, `clk`, `rst`, and `ena`. Its output port is `pwm_out`. Figure 2 is a schematic of the module.

`audio_pwm_generator` modulates the output by making a greater than comparison to a 12-bit counter.

We improved the quality of the PWM signal with a simple trick found in this [blog post](#): reversing the bits in the counter to generate the PWM signal. This improves the spacing of the pulses. This is best illustrated with an example. Luckily, Table 1 has an example of a 3 bit sample PWM module with a sample of `3'b100`.

Table 1: PWM generator with a sample of `3'b100`. Both the counter and reversed counter have the same number of high output cycles, but the reversed counter has more distribution among the pulses.

counter	out	counter_rev	out_rev
000	1	000	1

counter	out	counter_rev	out_rev
001	1	100	0
010	1	010	1
011	0	110	0
100	0	001	1
101	0	101	0
110	0	011	0
111	0	111	0

The PWM module takes a 12-bit sample from the `audio` port every 272 clock cycles. With a clock frequency of 12MHz, this yields a sample rate of $12000000/272 \approx 44.1\text{kHz}$, twice the highest pitch a human can hear.

You might be wondering how we can modulate a 12-bit sample in 272 clock cycles. The answer is, we can't. However, due the reversed counter, the output becomes a $\log_2(272) \approx 8.09$ bit approximation of the 12-bit sample.

Channel

The `channel` module is responsible for generating waveforms and adding effects to them. Its inputs are `clk`, `ena`, `rst`, `[11:0] pitch`, and `[1:0] waveform`. Its output is `[10:0] out`. Figure 3 is a schematic of the module.

`channel` is able to select between 4 different waveforms, shown in Table 2. It can generate frequencies in the from 5.7Hz to 23437.5Hz. the frequency generated is controlled from the `[11:0] pitch` input (0–4095) and is modeled by Equation 1.

Table 2: Waveform generated by channel based on `waveform` select input.

<code>[1:0] waveform</code>	Waveform
00	Square
01	Triangle
10	Sine
11	Sawtooth

$$f(x) = \frac{12MHz}{2 \cdot 256 \cdot (x + 1)} \quad (1)$$

The `channel` module contains an 8-bit counter. The counter increments at a rate defined by the `clock_divider` module and `pitch`. Its value represents the sample number of an 8-bit sample, which is fed into one of 4 `waveform generator`.

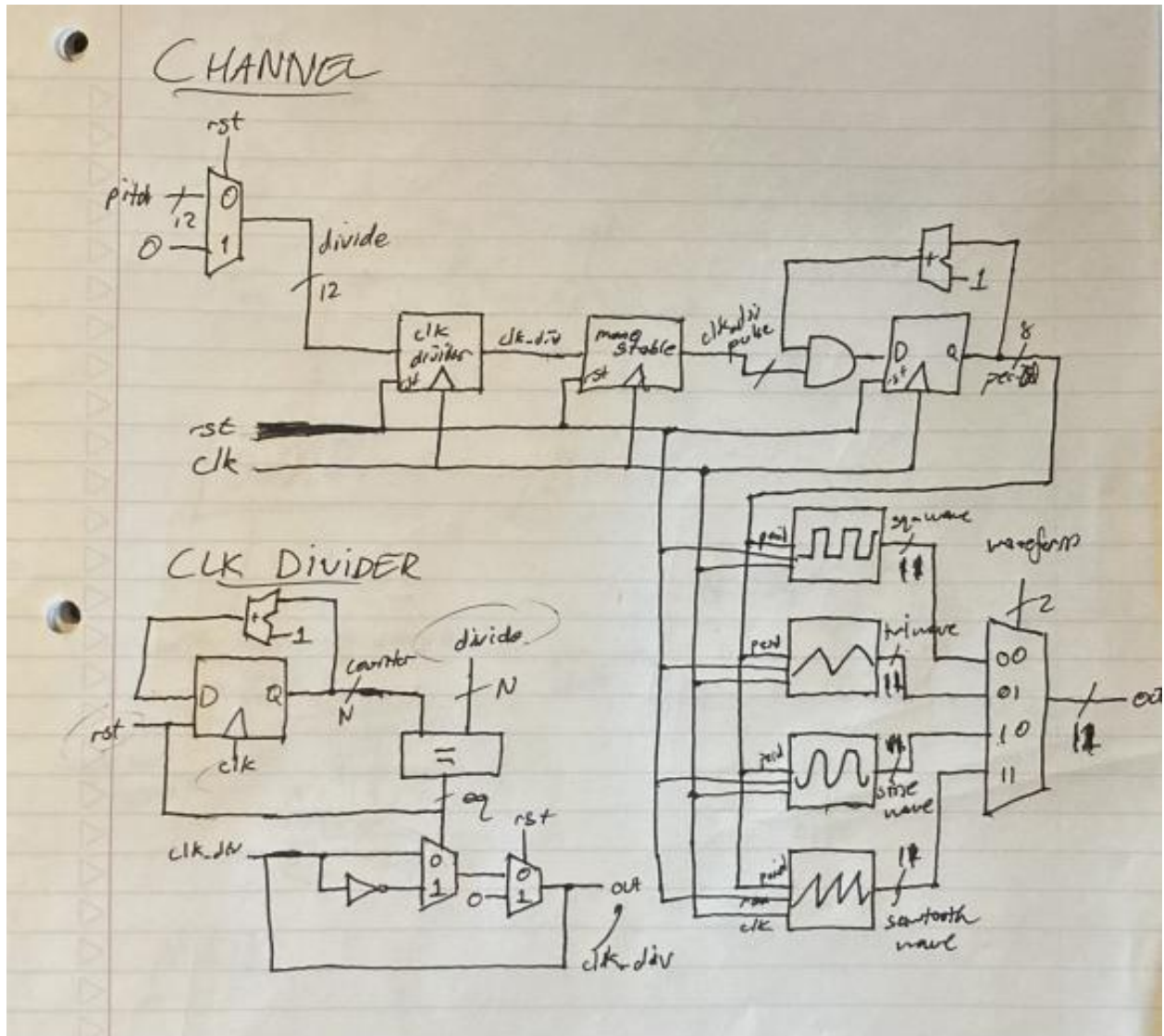


Figure 3: Schematic of channel

Clock Divider

The `clock_divider` module exists to slow the clock signal by a specified amount for generating audio waveforms. Its inputs are `clk`, `rst`, and 7:0 `divide` and its output is `clk_divided`.

`clock_divider` outputs a clock at a frequency defined by:

$$\text{output freq} = \frac{\text{input freq}}{2(\text{divide} + 1)}$$

Wave Generators

Each wave generator is a combinational logic block that takes an 8-bit input (from a `channels` period counter) and outputs an 11-bit value representing a waveform's sample.

`sq_wave_generator` outputs a square wave with the following CL:

```
always_comb square = (period[7]) ? -1 : 11'b0;
```

Alternatively, you could extend the most significant bit of the input instead of muxing it.

`tri_wave_generator` outputs a triangle wave with the following CL:

```
always_comb begin
    triangle = period[7] ? {~period[6:0], ~{4{period[0]}}}
                      : { period[6:0],  {4{period[0]}}};
end
```

`sine_wave_generator` outputs a sine wave from a lookup table defined as giant `case` statement.

`saw_wave_generator` outputs a sawtooth wave with the following CL:

```
always_comb saw = {period, {3{period[0]}}};
```

Debouncing

Since our synthesizer has keys with buttons, these buttons need to be debounced so that the signal inputted into the channel module is reliable. To do this, we created our own “bus debouncer,” which debounces all the buttons virtually simultaneously. It has a parameter `N` representing the number of buttons in the bus. Its inputs are `clk`, `rst`, and `bouncy_in[N-1:0]`, and its output is `debounced_out[N-1:0]`.

Before understanding how that works, first we implemented a 1-bit debouncer. The debounces FSM has four main states: `S_0`, `S_1`, `S_MAYBE_0`, and `S_MAYBE_1`. The two former states (`S_0` and `S_1`) are enabled when the debouncer knows the button's state, and the latter two states (`S_MAYBE_0` and `S_MAYBE_1`) are active when the debouncer is trying to figure out the state of the button.

To switch between the states, we need a set number of `BOUNCE_TICKS` to process how long to wait (i.e. how many clock cycles) to confirm the state of our button. Say the FSM is at `S_0`.

Once the button is pressed (goes HIGH), the state will change to `S_MAYBE_1`. To know if the button is actually staying pressed, we need to count up `BOUNCE_TICKS` number of clock cycles, and if the button state is still HIGH, we can then change to `S_1`. This means we need a counter (D flip flop) to count the number of clock cycles since changing states and a comparator to see when our counter is equal to `BOUNCE_TICKS`.

Using a `generate` block, we allowed for all the buttons in a bus to be debounced.

Monostable

We implemented a monostable for the button controlling the waveform mode. The reason for this is that the waveform mode changes for every press; however, we did not want to have the states cycle through every clock cycle as the user holds down the button. To make sure that holding down the waveform mode button counts as one button press (i.e. a press over one clock cycle), we use a monostable. Its inputs are `clk`, `rst`, and `button`, and its output is `out`.

Every clock cycle, the previous state of the button `prev` is updated to be the current state. (The exception is when the reset button is hit, in which case `prev` is set to 0). Once the button is released, the button will fall LOW while `prev` stays HIGH for one clock cycle. The following logic:

```
always_comb out = button & ~prev
```

ensures that the output goes high for that one clock cycle after release.

Wave Adder

The `wave_adder` adds up two 11-bit signals to output a 12-bit signal. It is a fairly simple module: both 11-bit signals have a 0 appended at the front to extend them both into 12-bit signals, and they are added together behaviorally. Its inputs are `channel1[10:0]` and `channel2[10:0]`, and its output is `out[11:0]`.

Get Waveform

Finally the `get_waveform` module is an FSM that outputs which waveform is currently selected. There are four states for each waveform: `S_SQUARE`, `S_TRIANGLE`, `S_SINE`, and `S_SAWTOOTH`. Whichever state is active determines the output of the module `waveform_out` as the 2-bit code of the waveform selected. (See Table 2.)

First, the incoming `waveform_button` signal is run through a monostable. This is to ensure that if the button is being held down, the module reads that as a singular button press (with the length of one clock cycle). Every clock cycle, the FSM checks to see if the button signal goes high (is pressed), and when it is, it cycles to the next state. When the module is reset, it defaults to `S_SQUARE` as its state.